
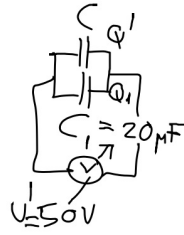


# Fizika I 7. gyakorlat

F1

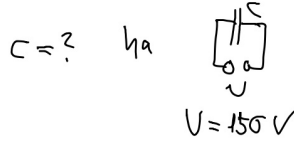

$$C = \frac{Q}{U} \rightarrow Q = CU$$

$$Q = Q' + Q_1$$

$$Q' = C \cdot U', \quad Q_1 = C_1 \cdot U'$$


$$Q = U' (C + C_1)$$

$$CU = (C + C_1)U'$$

$$C = \frac{C_1 U'}{U - U'} = \frac{20 \text{ nF} \cdot 50 \text{ V}}{100 \text{ V}} = 10 \text{ nF}$$

$$[C] = \frac{[Q]}{[U]} = \frac{C}{V} = F$$

F2

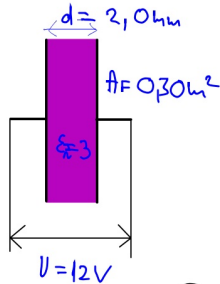


- $Q = ?$
- $\Delta \varphi = ?$
- $U = ?$  (ha kihúzzuk a szigetelést)
- $W_{\text{kihúzás}} = ?$

$$C = \epsilon_0 \epsilon_r \frac{A}{d} = 8,85 \cdot 10^{-12} \frac{F}{m} \cdot 3 \cdot \frac{0,30 \text{ m}^2}{2,0 \cdot 10^{-3} \text{ m}} = 3,98 \cdot 10^{-9} F \approx 4 \text{ nF}$$

a)  $Q = CU = 4 \text{ nF} \cdot 12V = 48 \text{ nC}$

b) egy lemeze Gauss t.

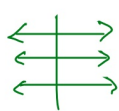

diédzshelyben  $E_{ind} = -\frac{\sigma_{ind}}{\epsilon_0 \epsilon_r}$

konduktóra valószínű

$$E_0 = \frac{\sigma}{\epsilon_0}$$

$$E = E_0 + E_{ind} = \frac{1}{\epsilon_0} \left( \sigma - \frac{\sigma_{ind}}{\epsilon_r} \right)$$

$$\text{de } E = \frac{E_0}{\epsilon_r} \Rightarrow \frac{E_0}{\epsilon_r} = \frac{1}{\epsilon_0} \left( \sigma - \frac{\sigma_{ind}}{\epsilon_r} \right) \Rightarrow \frac{\sigma}{\epsilon_r \epsilon_0} = \frac{1}{\epsilon_r} \left( \sigma - \frac{\sigma_{ind}}{\epsilon_r} \right)$$

$$\sigma_{ind} = \epsilon_r \cdot \sigma \left( 1 - \frac{1}{\epsilon_r} \right) = \sigma (\epsilon_r - 1)$$

$$\sigma_{ind} = \sigma (\epsilon_r - 1) = \epsilon_0 \frac{U}{d} (\epsilon_r - 1) = 8,85 \cdot 10^{-12} \frac{F}{m} \cdot \frac{12V}{2 \cdot 10^{-3} \text{ m}} \cdot 2 = 1,06 \cdot 10^{-7} \frac{C}{m^2}$$

$$\sigma = \epsilon_0 E = \epsilon_0 \frac{U}{d}$$

$$\frac{F}{m} \cdot \frac{V}{m} = \frac{C \cdot V}{m^2} = \frac{C}{m^2}$$

c) ha nincs szigetelés  $\Rightarrow C' = \epsilon_0 \frac{A}{d} = \frac{C}{\epsilon_r}$


$$U' = \frac{Q}{C'} = \epsilon_r \frac{Q}{C} = 3 \cdot 12V = 36V$$

$$d) W = \sum_{\text{váltakozó}} - \varepsilon_{\text{csatlakozás}} = \frac{1}{2} C U^2 - \frac{1}{2} C U^2$$


$$= \frac{1}{2} C \left( \frac{U^2}{\varepsilon_r} - U^2 \right) = \frac{1}{2} \cdot 3,98 \cdot 10^{-9} \text{ F} \cdot \left( \frac{36^2}{3} - 12^2 \right) \text{ V}^2 = 5,74 \cdot 10^{-7} \text{ J}$$

$F \cdot V^2 = \frac{C}{V} \cdot V^2 = C V = Q$


F3

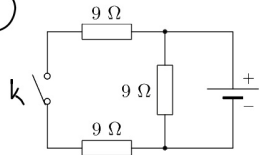

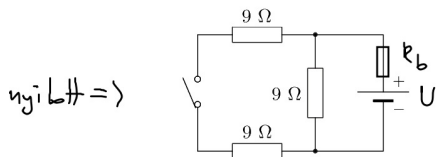Ha k nyitva 400mA a telep ágában,  
zárva 500mA  
 $R_b = ?$


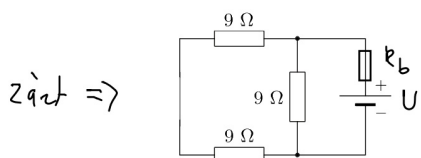
$$I_1 = \frac{U}{R_b + 9\Omega} \Rightarrow U = I_1 (R_b + 9\Omega)$$



$$R = \frac{1}{\frac{1}{9} + \frac{1}{9}} = \frac{1}{\frac{2}{9}} = \frac{9}{2} = 4,5\Omega$$


(ohm)

$$I_2 = \frac{U}{R + R_b} = \frac{R_b + 9\Omega}{R + R_b} \cdot I_1$$

$$R I_2 + R_b I_2 = R_b I_1 + 9\Omega \cdot I_1$$

$$R_b = \frac{9\Omega \cdot I_1 - R \cdot I_2}{I_2 - I_1} = \frac{9 \cdot 400 - 4,5 \cdot 500}{100} = \frac{3600 - 2250}{100} = 13,5\Omega$$

F4

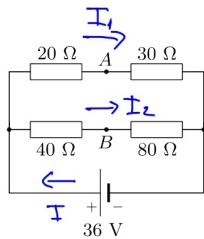

a)  $U_{AB} = ?$

b)  $R = ?$  a 30Ω helyett, hogy  $U_{AB} = 0$  legyen

a)  $U_{AB} = I_1 \cdot 20\Omega - I_2 \cdot 40\Omega \stackrel{!}{=} 0$

$$I_1 \cdot (20 + 30) = I_2 (40 + 80) \Rightarrow 5 I_1 = 12 I_2$$

$$I = \frac{U}{R_x} = \frac{36}{\frac{1}{\frac{1}{20+30} + \frac{1}{40+80}}} = 36 \cdot \frac{50 + 120}{50 \cdot 120} = 36 \cdot \frac{17}{600} = 1,02 \text{ A}$$

$$I_1 + I_2 = I$$

$$5 I_1 = 12 I_2$$

=>

$$I_1 + \frac{5}{12} I_1 = I$$

$$I_1 = \frac{12}{17} I = \frac{36 \cdot 12}{600} = 0,72 \text{ A}$$

$$I_2 = I - I_1 = 0,3 \text{ A}$$

$$U_{AB} = 20\Omega \cdot 0,72A - 40\Omega \cdot 0,3A = 2,4V$$

b)  $U_{AB} = 0$  heißt  $R$ -et immer


$$U_{AB} = 0 \Rightarrow \begin{cases} I_1 \cdot R = I_2 \cdot 80\Omega \\ (20\Omega + R)I_1 = 120\Omega I_2 \end{cases} \Rightarrow \frac{20+R}{R} = \frac{120}{80}$$

$$20 + R = 1,5R$$

$$20 = 0,5R$$

$$R = 40\Omega$$

F5

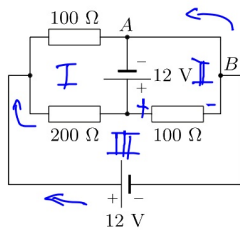


a)  $I_{200\Omega} = ?$

b)  $I_{AB} = ?$

c)  $P = ?$


d)  $I$  -  $U$  Kurven:  $U_{100\Omega} = 12V$   
 $U_{200} + U_{100} = 12V$  }  $U_{200} = 0V$   
 $\downarrow$   
 $I_{200\Omega} = 0A$

e)  $U_{AB} = 0V \Rightarrow I_{AB} = 0$

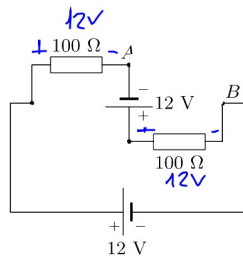

f)  $I_{100\Omega} = \frac{12V}{100\Omega} = 0,12A \Rightarrow P_{100\Omega} = I^2 \cdot R = 1,44W$   
 $P = 2 \times P_{100\Omega} = 2,88W$

F6

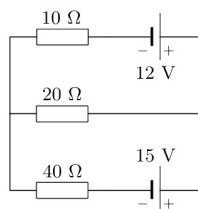

a) Kirchhoff'sche

b) Superposition'sche


a)

$$-12 + I_1 \cdot 10 + 20(I_1 + I_2) = 0 \Rightarrow 30I_1 + 20I_2 = 12$$

$$20 \cdot (I_1 + I_2) + 40 \cdot I_2 - 15V = 0 \Rightarrow 20I_1 + 60I_2 = 15$$

$$I_1 = \frac{12}{30} - \frac{2}{3} I_2$$

b)

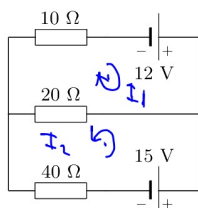


$$20 \cdot \frac{12}{30} - \frac{40}{3} I_2 + 60 I_2 = 15$$

$$\frac{140}{3} I_2 = 7$$

$$I_2 = \frac{21}{140} = \underline{0,15 \text{ A}}$$

$$I_1 = \frac{2}{5} - \frac{2}{3} I_2 = 0,4 - 0,1 = \underline{0,3 \text{ A}}$$

10 Ω	0,3 A
20 Ω	0,45 A
40 Ω	0,15 A

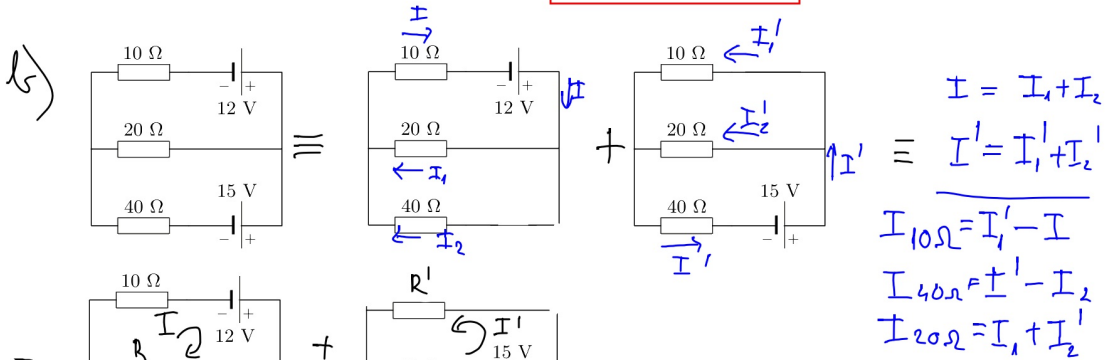


$$I = I_1 + I_2$$

$$I' = I'_1 + I'_2$$

$$I_{10\Omega} = I'_1 - I$$

$$I_{40\Omega} = I'_2 - I_2$$

$$I_{20\Omega} = I_1 + I'_2$$

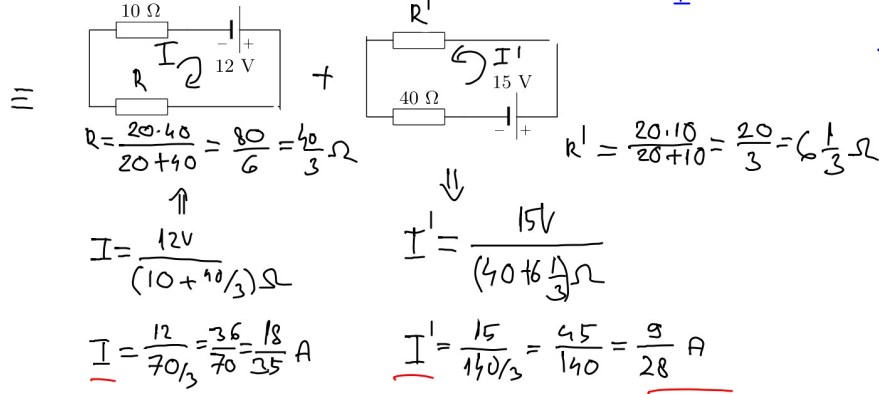

$$I = I_1 + I_2 \quad \left. \begin{array}{l} I_2 = \frac{I}{3} = \frac{6}{35} \text{ A} \\ I_1 = \frac{12}{35} \text{ A} \end{array} \right\}$$


$$I' = I'_1 + I'_2 \quad \left. \begin{array}{l} I'_2 = \frac{I'}{3} = \frac{3}{28} \text{ A} \\ I'_1 = \frac{6}{28} \text{ A} = \frac{3}{14} \text{ A} \end{array} \right\}$$


$$I_{10\Omega} = \frac{3}{14} - \frac{18}{35} = -0,3 \text{ A}$$

$$I_{20\Omega} = \frac{12}{35} + \frac{3}{28} = 0,45 \text{ A}$$


$$I_{40\Omega} = \frac{9}{28} - \frac{6}{35} = 0,15 \text{ A}$$

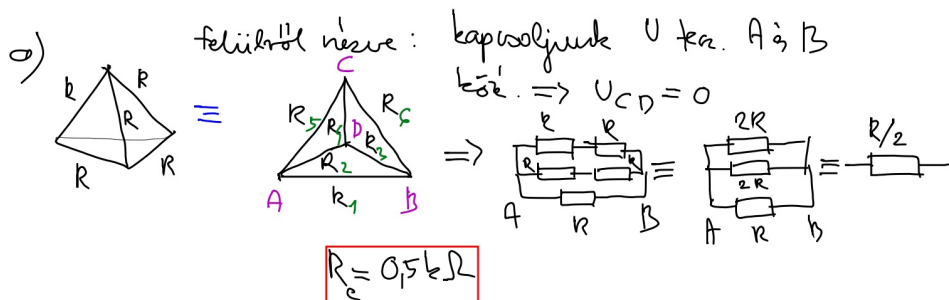F7) 12Ω os húzaldalak a) tetraéder  $R_e = ?$  v 2 csúcs pont között  
 b) kocka  $R_e = ?$  testátló két végén



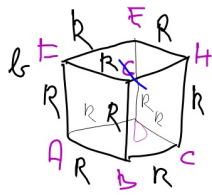

$$R_{AH} = ?$$

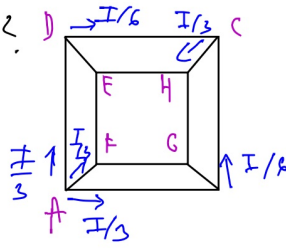


$$U_{AH} = R_{AH} \cdot I$$

$$U_{AH} = R \cdot \frac{I}{3} + R \cdot \frac{I}{6} + R \cdot \frac{I}{3} = \frac{5}{6} RI$$



$$R_{AH} = \frac{5}{6} I$$

FS

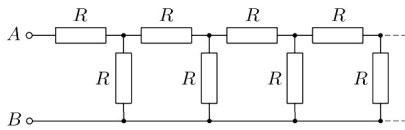

Tegyük fel, hogy az eredő  $R_E$ !

Mivel  $\infty$

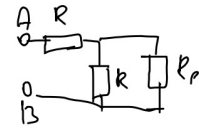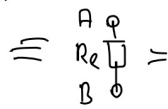

$$R_{AB} = R_E \quad \Rightarrow \quad R_{AB} = R + \frac{1}{\frac{1}{R} + \frac{1}{R_E}} = R + \frac{R E}{R_E + R}$$

$$R_E = R + \frac{R E}{R_E + R}$$

$$R_E^2 + R E = R E + R^2 + R E$$

$$R_E^2 - R \cdot R_E - R^2 = 0$$

$$R_{E1,2} = \frac{R \pm \sqrt{R^2 + 4R^2}}{2} = R \frac{1 \pm \sqrt{5}}{2} \quad R \rightarrow R_E > 0$$

$$R_E = \frac{1 + \sqrt{5}}{2} R$$